

PERFORMING THE STARTER SYSTEM VOLTAGE DROP TEST

Tools needed:

1. DVOM- Digital Volt/Ohm meter
2. Extension jumper lead

Step 1: Connect the DVOM between the battery positive post and the main positive connection to the starter motor. Measure the voltage drop during cranking on the voltage side of the starter circuit.

measurement

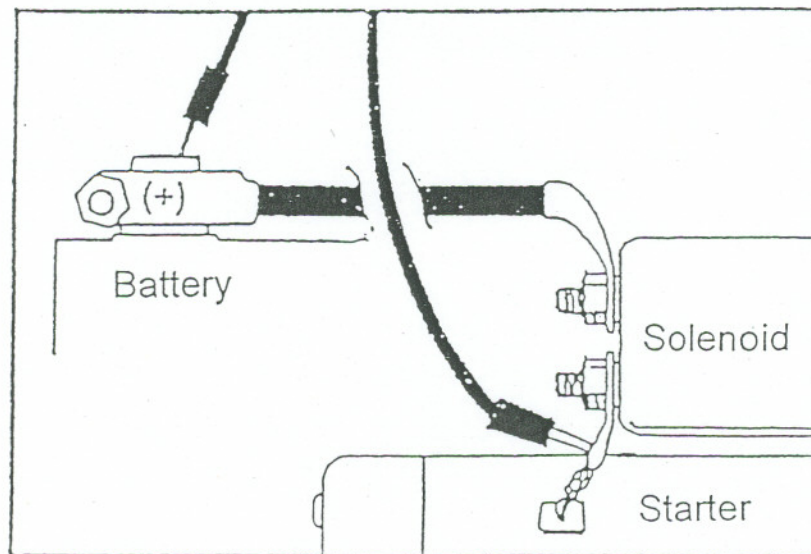


Figure 1: Checking the positive side of Starter Motor Circuit

Step 2: Connect the DVOM between the battery negative post and a clean spot on the starter motor housing. Take a measurement during cranking. This tests the voltage drop on the **negative** side of the circuit.

measurement

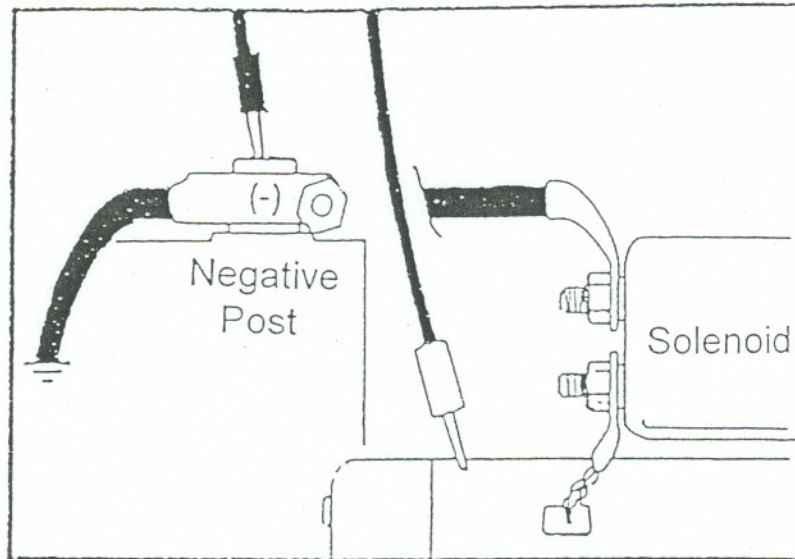


Figure 2: Check at a clean spot on the starter housing

Step 3: Connect the DVOM leads as shown. Test the connection between battery positive post and the battery positive cable terminal end **while cranking**.

measurement

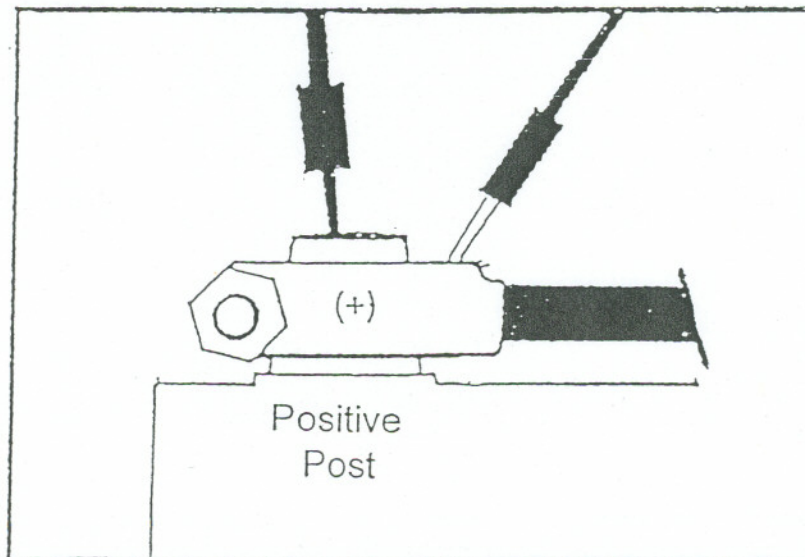


Figure 3: Checking voltage drop between the positive battery post and the

Step 4: Next test the positive battery cable for voltage drop. Connect the DVOM as shown to take a reading across the positive battery cable.

_____ measurement

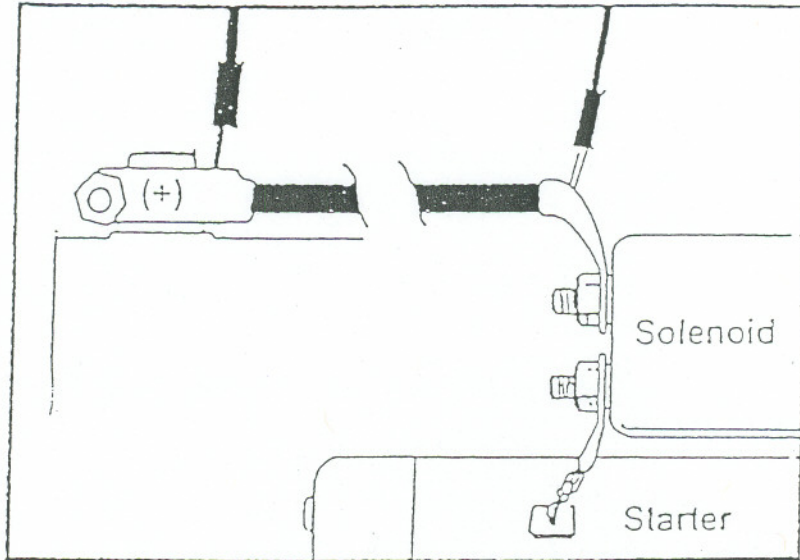


Figure 4: Checking the positive battery cable resistance using a voltage drop test.

Step 5: Now check the connection between the battery positive cable and the solenoid while cranking the engine. You are measuring the terminal end and connection.

_____ measurement

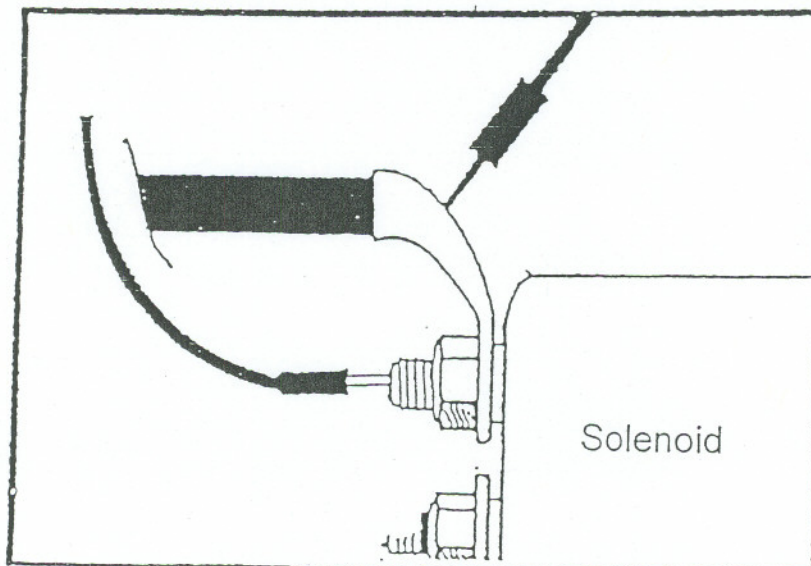


Figure 5: Checking the voltage drop between the positive battery cable lug and the solenoid stud.

Step 6: Clean and suspect terminals and replace any faulty components. Then, re-check the system by completing Steps 1 & 2 again.

_____ measurement

REMEMBER:

All tests are made with the engine cranking.

The rule of thumb is that each termination in the circuit should have a voltage drop of no greater than 0.2 volts.